

Assignment : 02. (By Manan Madan
201801C3087)


Ques: 01 What is an inverter? List few industrial applications of it.

Ans: An inverter is an electrical device, & it is capable of changing a DC current to an AC current at a given frequency as well as voltage. The AC power can be supplied to homes & industries using the public utility otherwise power grid, the alternating power system of the battery can store only DC power.

In some situation like when the DC voltage is low, then we cannot use the low DC voltage in a home appliance. So due to this reason, an inverter can be used whenever we utilize solar power panel.

Types of Inverter:

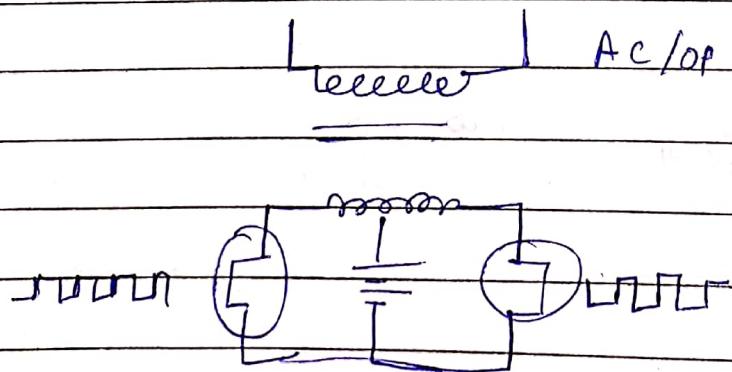- Single phase Inverter
- Three phase Inverter



Applications:

- used as on UPS (uninterruptible power supplies)
- used as standalone inverters.
- used in Solar power systems
- used in Centrifugal fans, pumps, mixers, extruders, test stands - and web handling equipment.


Ques: what are the purpose of connecting diodes in antiparallel with thyristors in inverter circuits?

Ans: when a diode got connected with thyristor or SCR then it became unipolar switch. whenever a diode placed antiparallel to any switching device it became unipolar so when diode connected its voltage drop on forward biased will become reverse voltage drop for SCR during its off-time & voltage drop for power diode is between 0.8 - 1 volt so reverse power loss become less for SCR as initially we may considering some bulky commutation circuit with voltage drop more than 1 volt so power loss more in other then antiparallel diode.

by using antiparallel diode power loss decreases & turn-off time increases.

Ques: Q3 Describe the working of a single phase half bridge inverter, what is its main drawback? Explain how this drawback is overcome.


Ans:

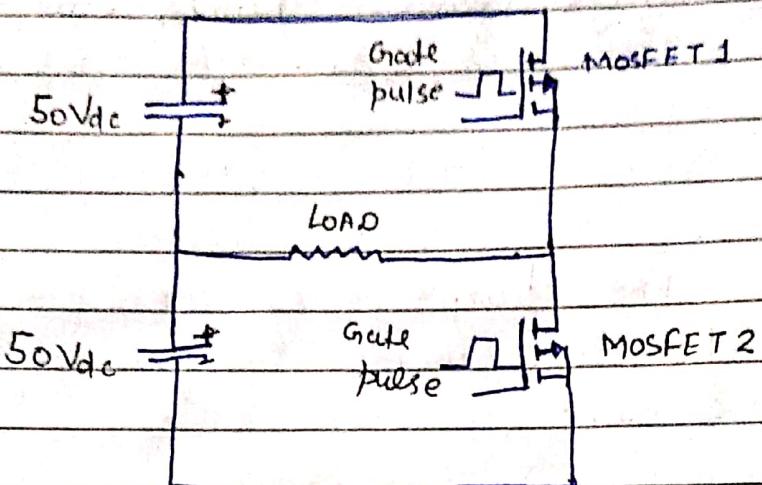


Half Bridge inverter

This type of Inverter requires two power electronics switches (MOSFET). The MOSFET or IGBT is used for switching purpose.

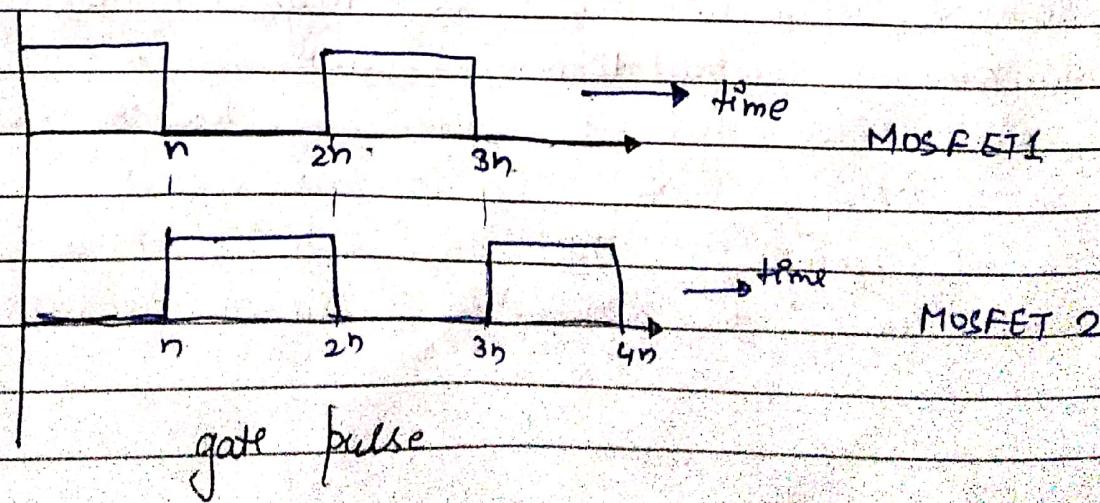As shown in circuit diagram, $V_{DC} = 100V$. This source is divided into two equal parts.



start to o/p freq., ON time and OFF time of MOSFET is decided & gate pulse are generated. we need 50Hz AC power, so the time period of one cycle ($0 < t < 2\pi$) is 20 msec, from fig., MOSFET-1 is triggered for first half cycle ($0 < t < \pi$) and during this time period, current will flow in direction shown in below figure & half cycle of AC o/p is completed. The current from the load is right to left & load voltage is equal to $+V_{dc}/2$.

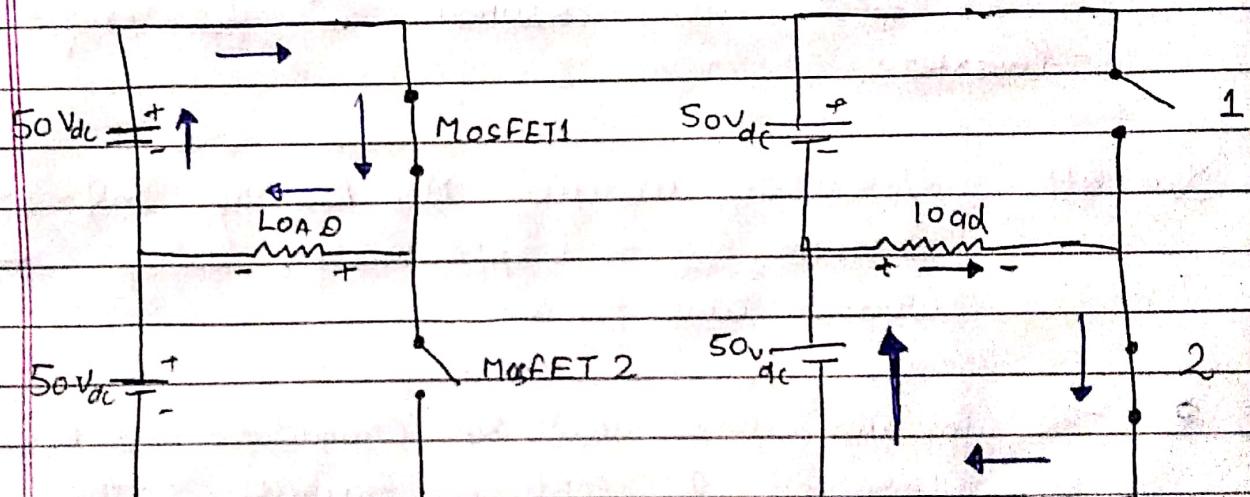

In second half cycle ($\pi < t < 2\pi$), the MOSFET-2 is triggered and lower voltage source is connected with the load. The current from the load is left to right dir? & load voltage is equal to $-V_{dc}/2$.

Ques. 03:

the main drawback is source utilization factor when compared to full bridge inverters.


It don't utilise the total source voltage at a time.

In every half cycle, voltage across the load is only half of source voltage i.e., $V_s/2$ whereas in full bridge inverter in every half cycle total voltage V_s appears across the load. So the power consumed by load is half of what is consumed in full bridge inverter.

Ques. 04 Describe modified Mc Murray half-bridge inverter with appropriate voltage & current wave forms.

→ The inverter uses auxiliary commutation scheme to turn off a conducting thyristor. The main inverter circuit is similar to the half-bridge circuit, except that it uses Thyristors T_1 & T_2 in place of commutated switches S_1 & S_2 . The commutation circuit consists of ~~one~~ auxiliary thyristors TA_1 & TA_2 along with anti-parallel diodes DA_1 & DA_2 , Commutating elements L & C, and clamping resistance R. To transfer current from T_1 to T_2 , TA_1 is triggered and to transfer current from

T_2 to T_1 T_{A21} is triggered.

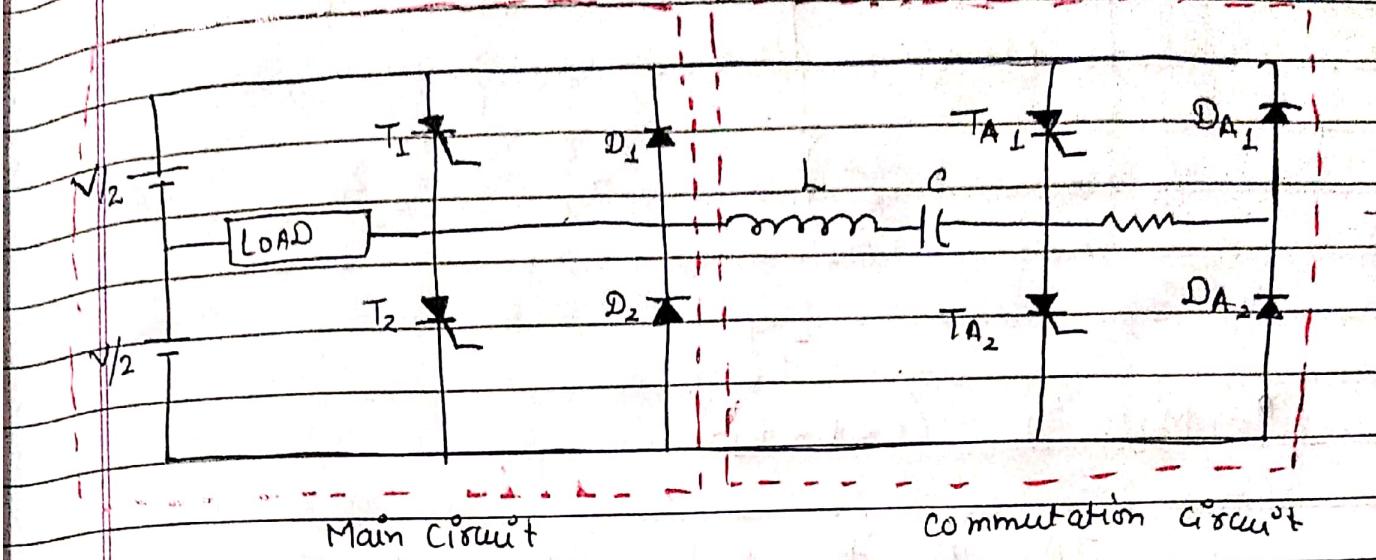


- Circuit of modified Mc Murray half-bridge Inverter

For the sake of simplification, it is assumed that all the devices and circuit elements are ideal. Moreover, it is assumed that the load is highly inductive so that the load current remains constant during commutation interval. The operation is divided into 8-modes.

Thick lines show conducting part & non-conducting parts are shown by dotted lines.

- Mode 01 ($t < 0$)

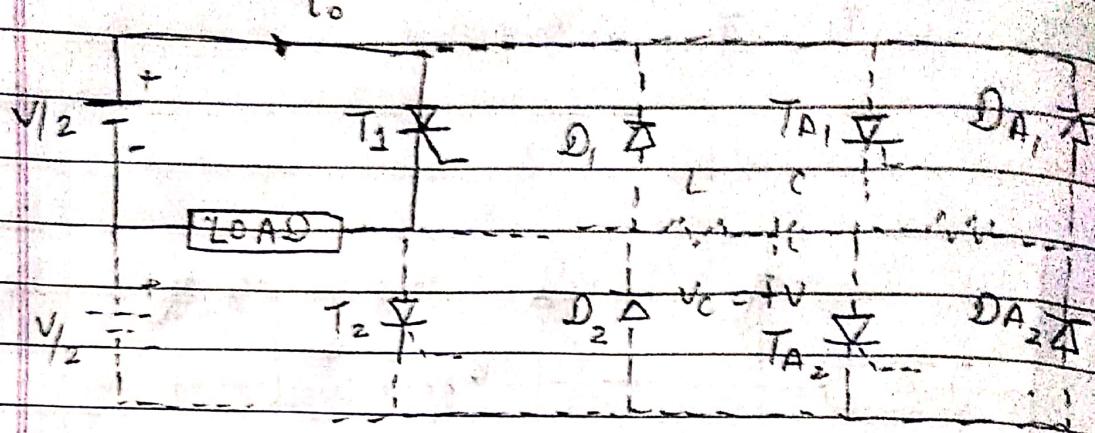
In this mode main thyristor T_1 conducts and a constant positive load current (I_0) flows. The load voltage is +ve & the capacitor is charged up to $+V$.



• Mode II ($t_1 < t < t_2$)


T_{A1} is triggered at $t = 0$ to Commutate T_1

$$i_{T_1} = I_o - i_c$$

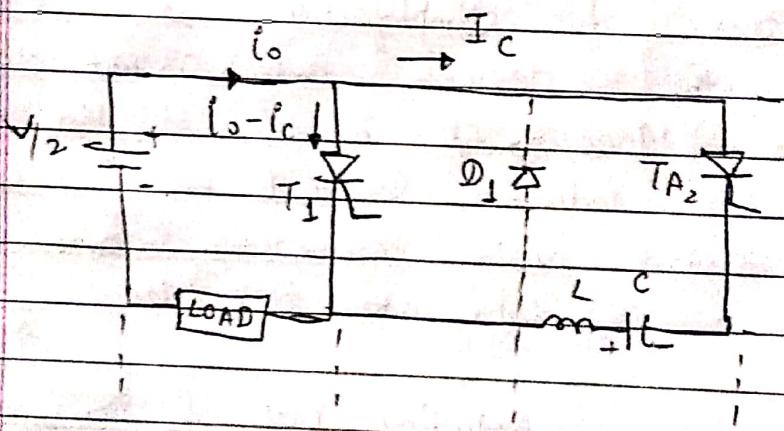


• Mode III ($t_2 < t < t_3$)

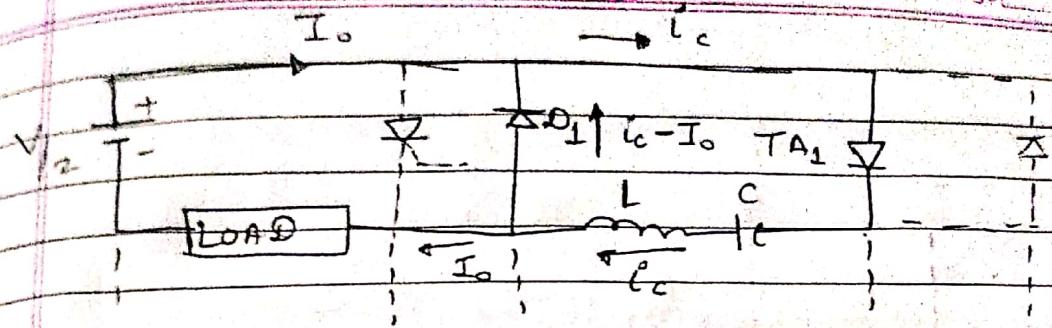As the resonating current i_c becomes higher than the load current (I_o), the surplus current ($i_c - I_o$) flows through the diode D_1 .



Mode - IV ($t_2 < t < t_3$)

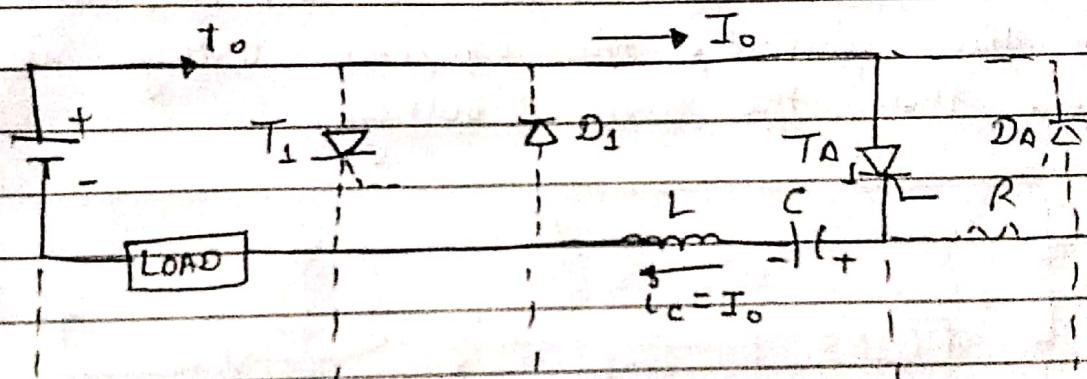
when D_1 turns off at the end of mode - III, the capacitor is charged in reverse direction by the const. load current I_0 during this interval, the voltage across diode D_2 , V_{D2} is equal to $(V_c - V)$.



Mode V ($t_3 < t < t_4$)


when D_2 turns on, I_0 is shared by D_2 & C . as $i_c = i_{D2}$, $i_{D2} = i_0$ which is equal to $I_0 - i_c$

dotted

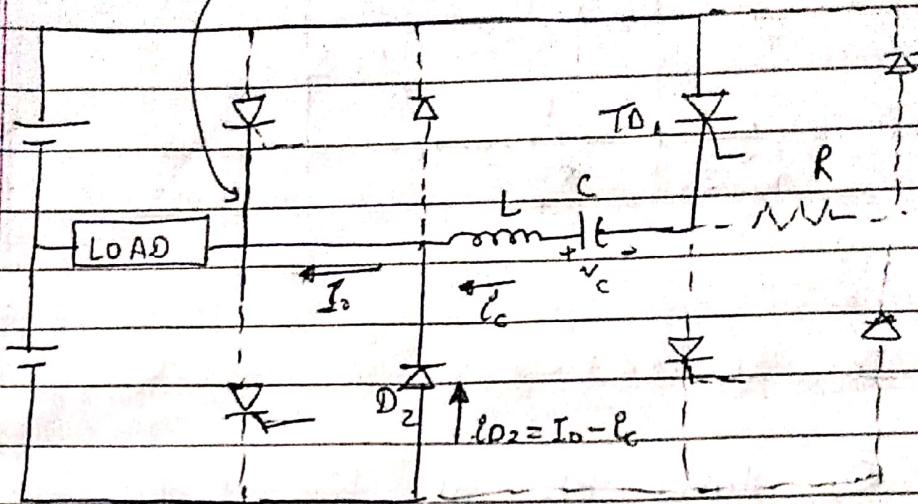


• Mode VI ($t_4 < t < t_5$)

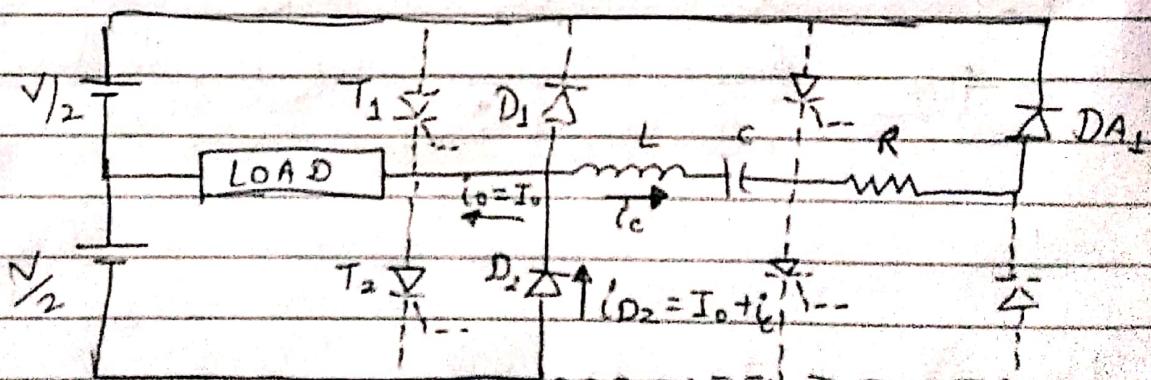as i_c tries to reverse at t_4 , D_{A1} turns on.
At this instant, the capacitors voltage is
more than the source voltage.




Mode VII ($t_5 < t < t_6$)

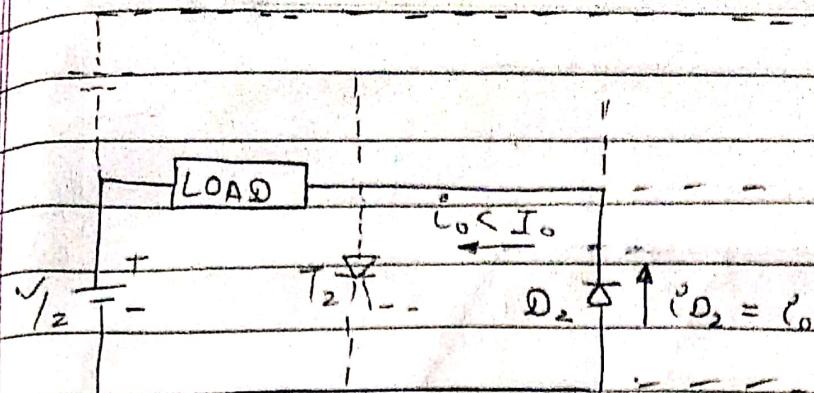During this interval, i_o flows through D_2 and the lower source.




• Mode VII ($t > t_6$)

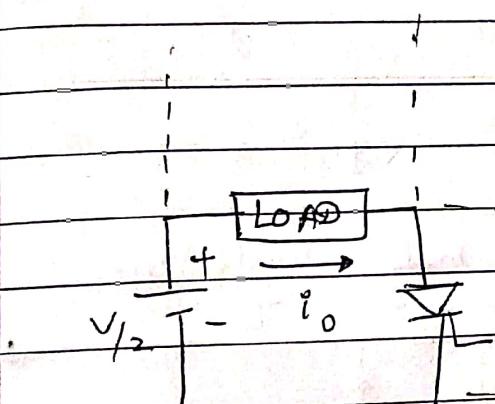When D_2 turns off, T_2 which is already receiving the gate signal turns on. It conducts and the -ve load current, raises to become equal to I_0 at $t=t_7$




Waveform

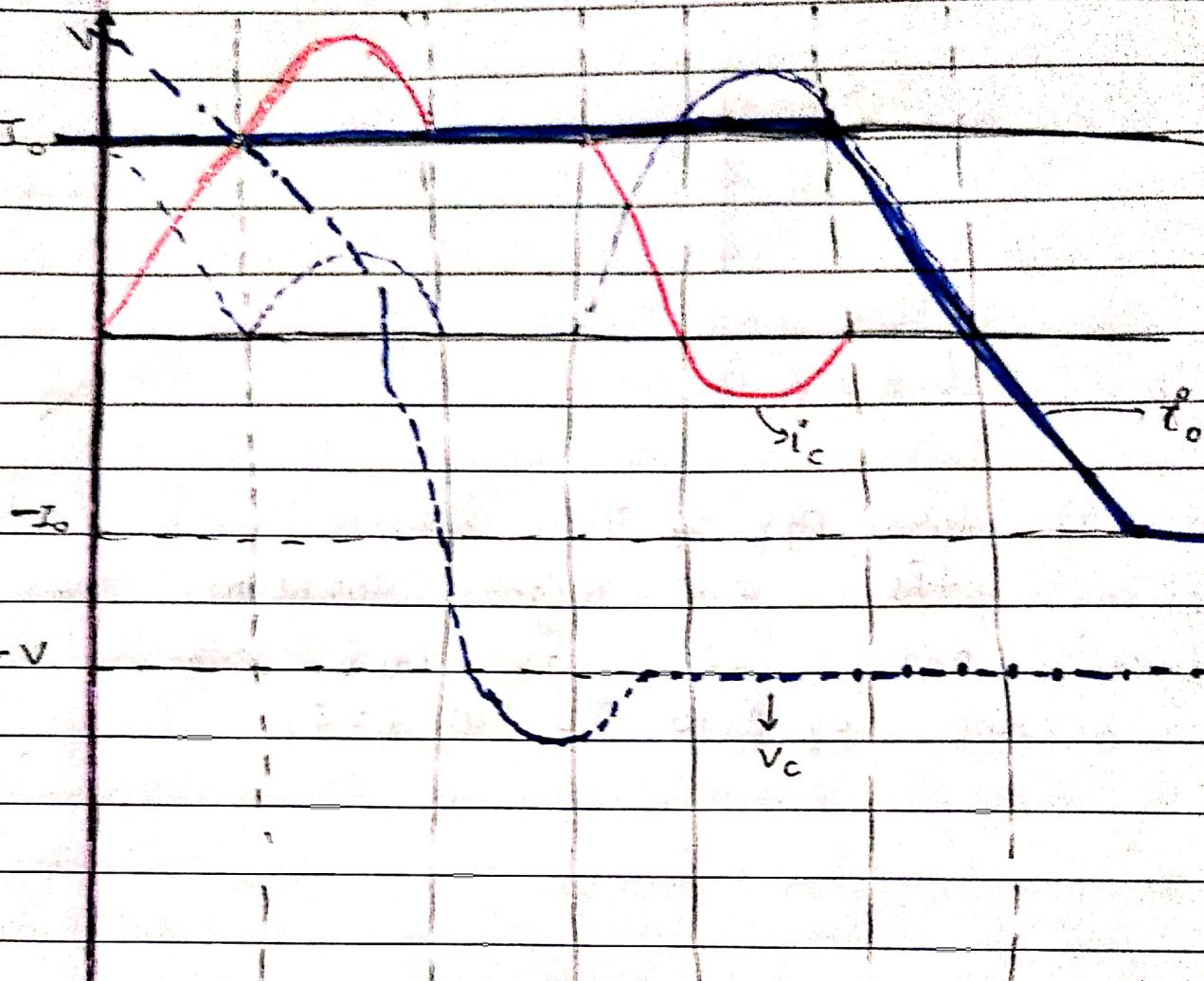


mode I	mode II	mode III	mode IV	mode V	mode VI	mode VII	mode VIII
Cond. I_1	T_1, TA_1	D_1, TA_1	TA_1	TA_2, D_2	DA_1, D_2	D_2	T_2
devices	D_1 , ON						
	T_1 off	D_1 off	D_2 on	TA_1 off	DA_1 off	D_2 off	T_2 on


Ques 05 Describe the modified Mc Murray Beddoes half bridge single phase inverter with relevant voltage & current waveforms. Also, explain advantages of it over modified Mc Murray half bridge inverter.

Diagram

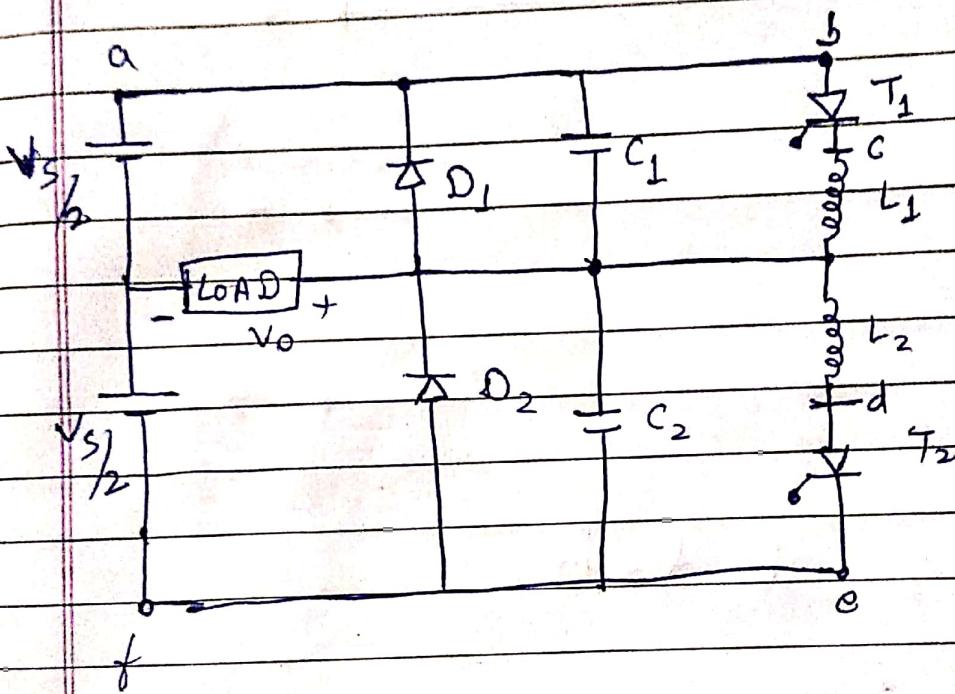


Mode 1 : before $t=0$

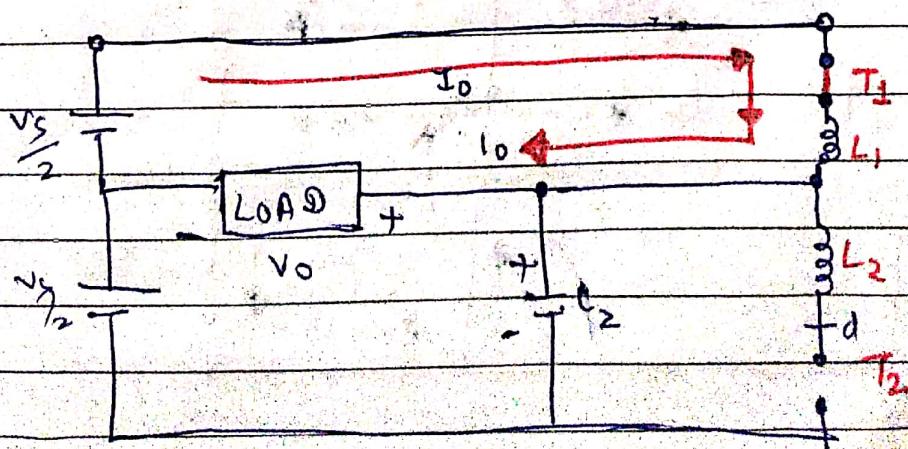

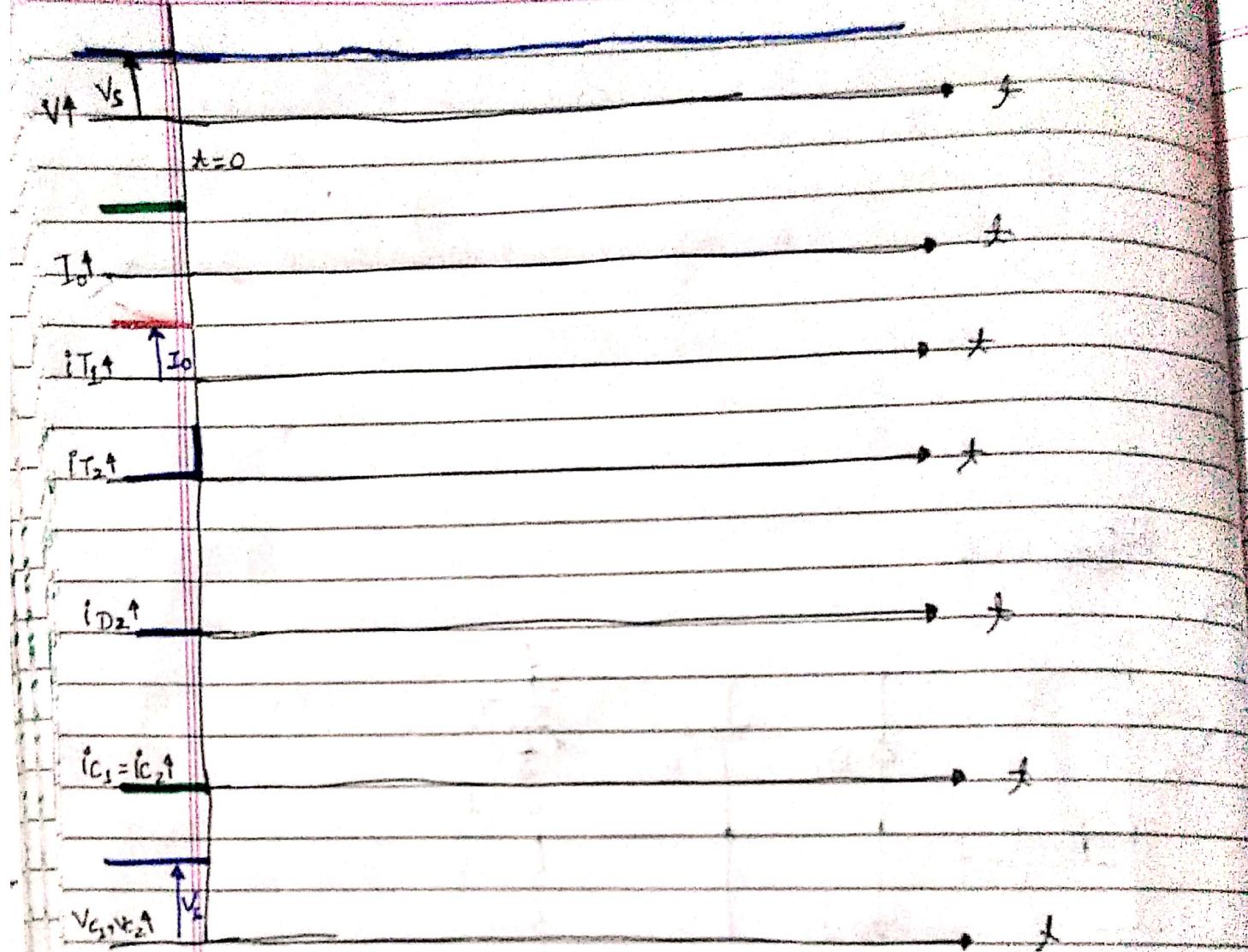


Mode : 02 at $\lambda = 0$

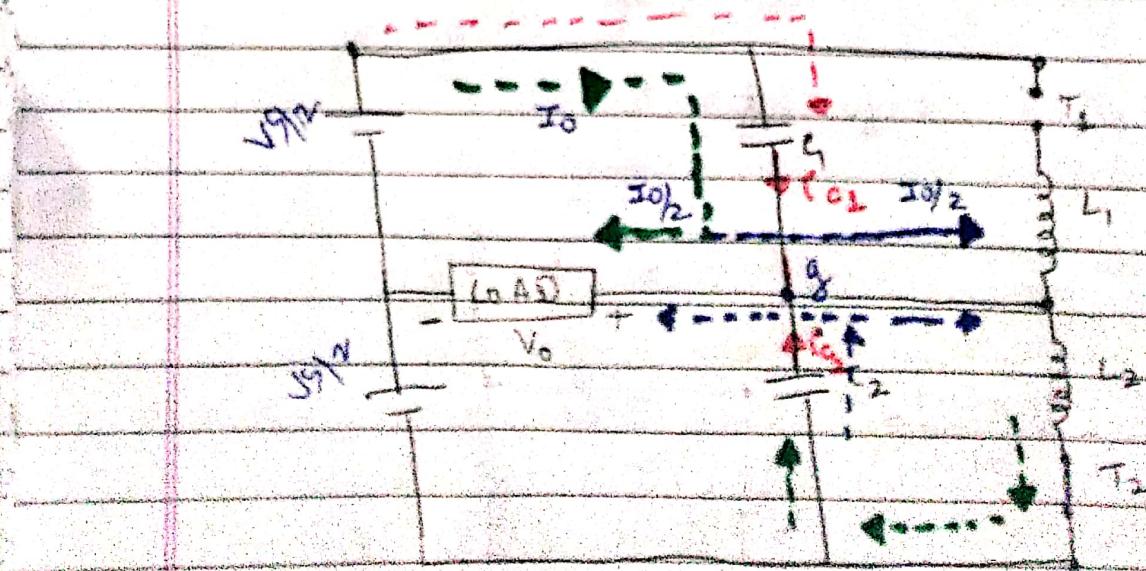

KVL at node g


$$i_{C_1} + i_{C_2} = I_0 + I_m \quad , \quad i^{\circ}C_1 = i^{\circ}C_2 = I_0 + \cancel{I_m}$$

$$\rightarrow A + \frac{1}{f} < f_1$$

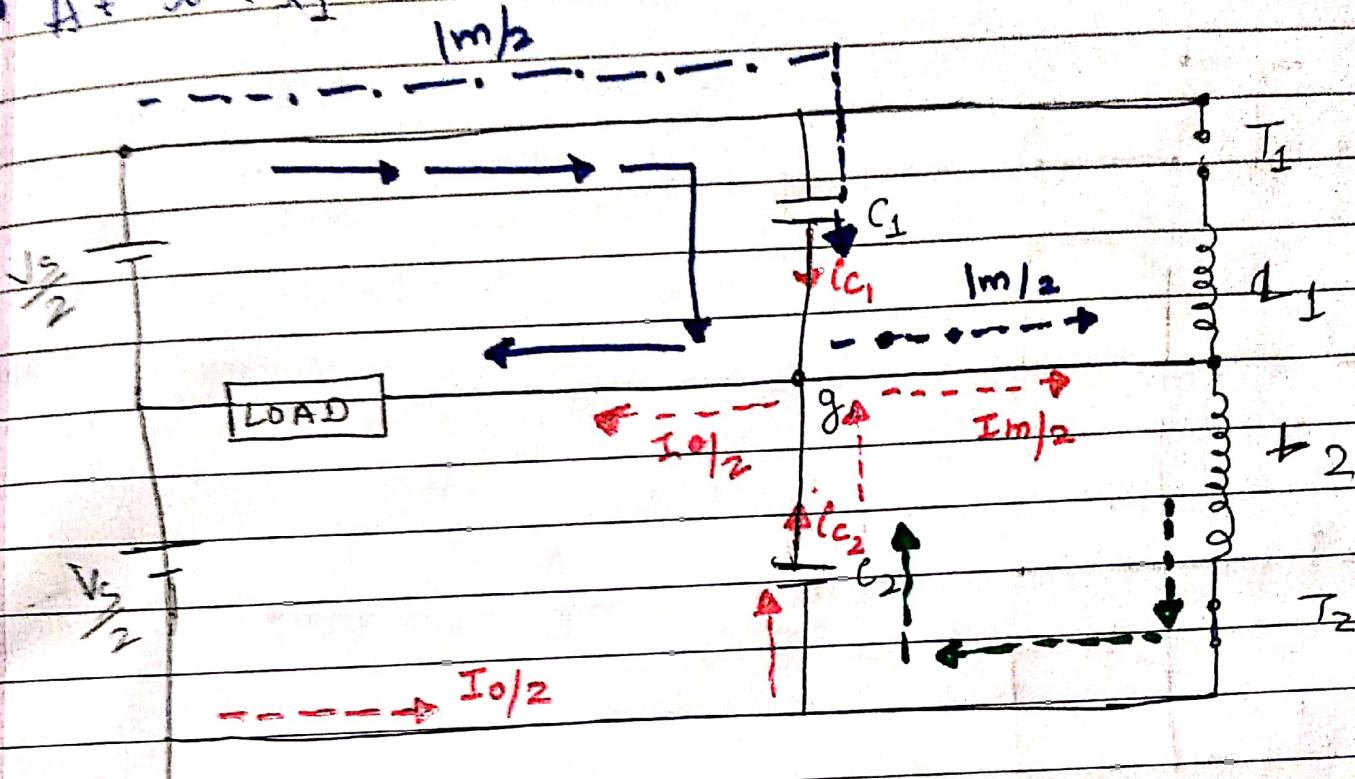


KCL at node g


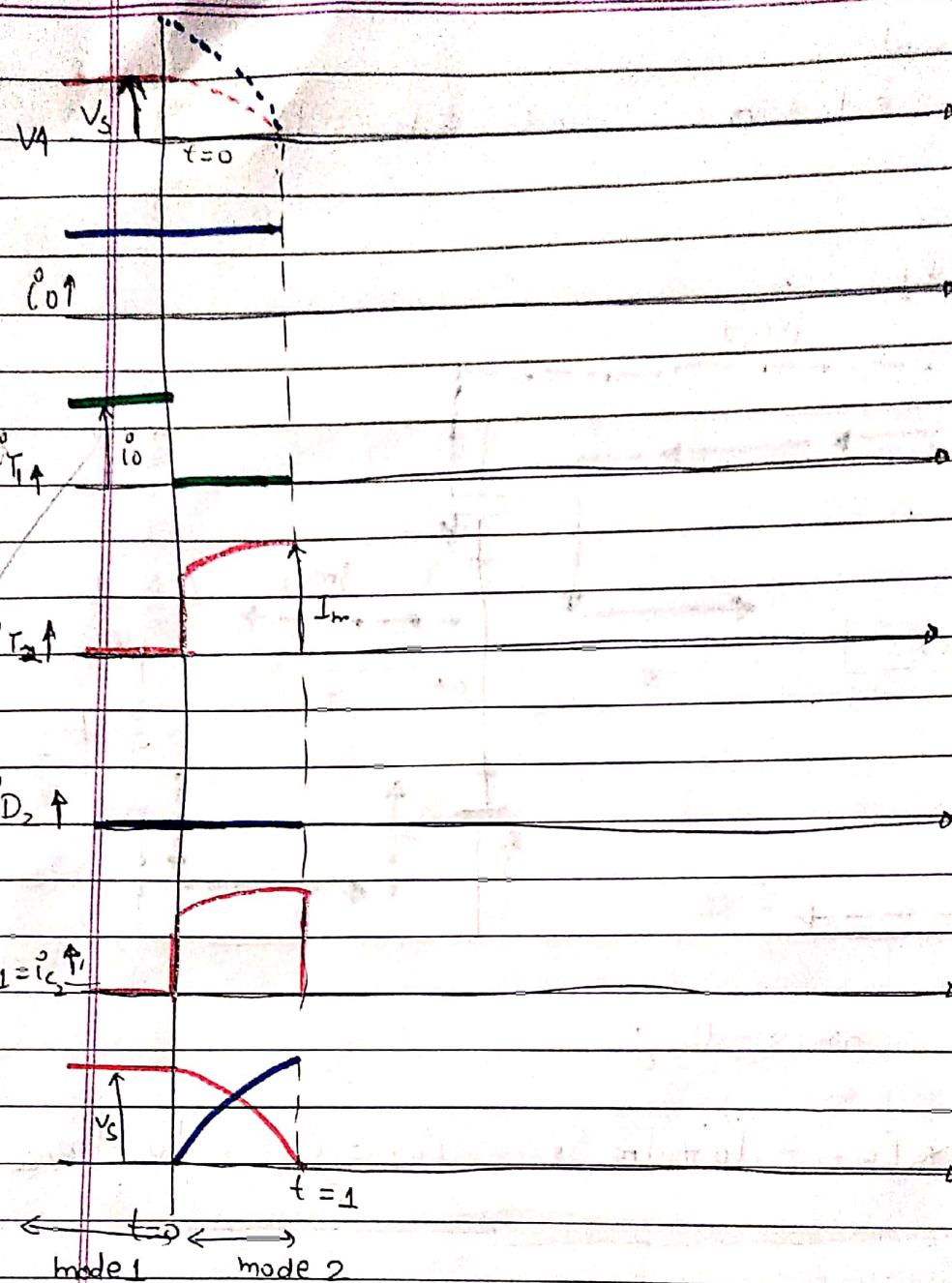
$$i^{\circ}C_1 + i^{\circ}C_2 = I_0 + I_m \quad , \quad i^{\circ}C_1 = i^{\circ}C_2 = I_0 + I_{m/2}$$



• Mode 3 at t_1

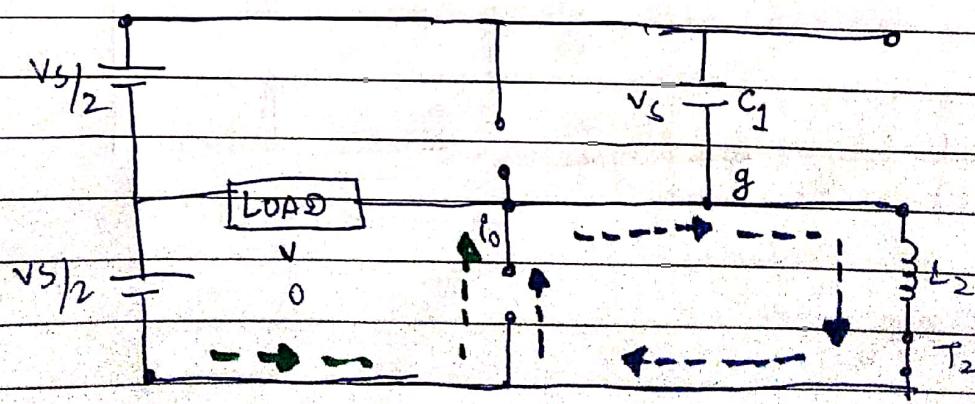


• Mode 3: 04

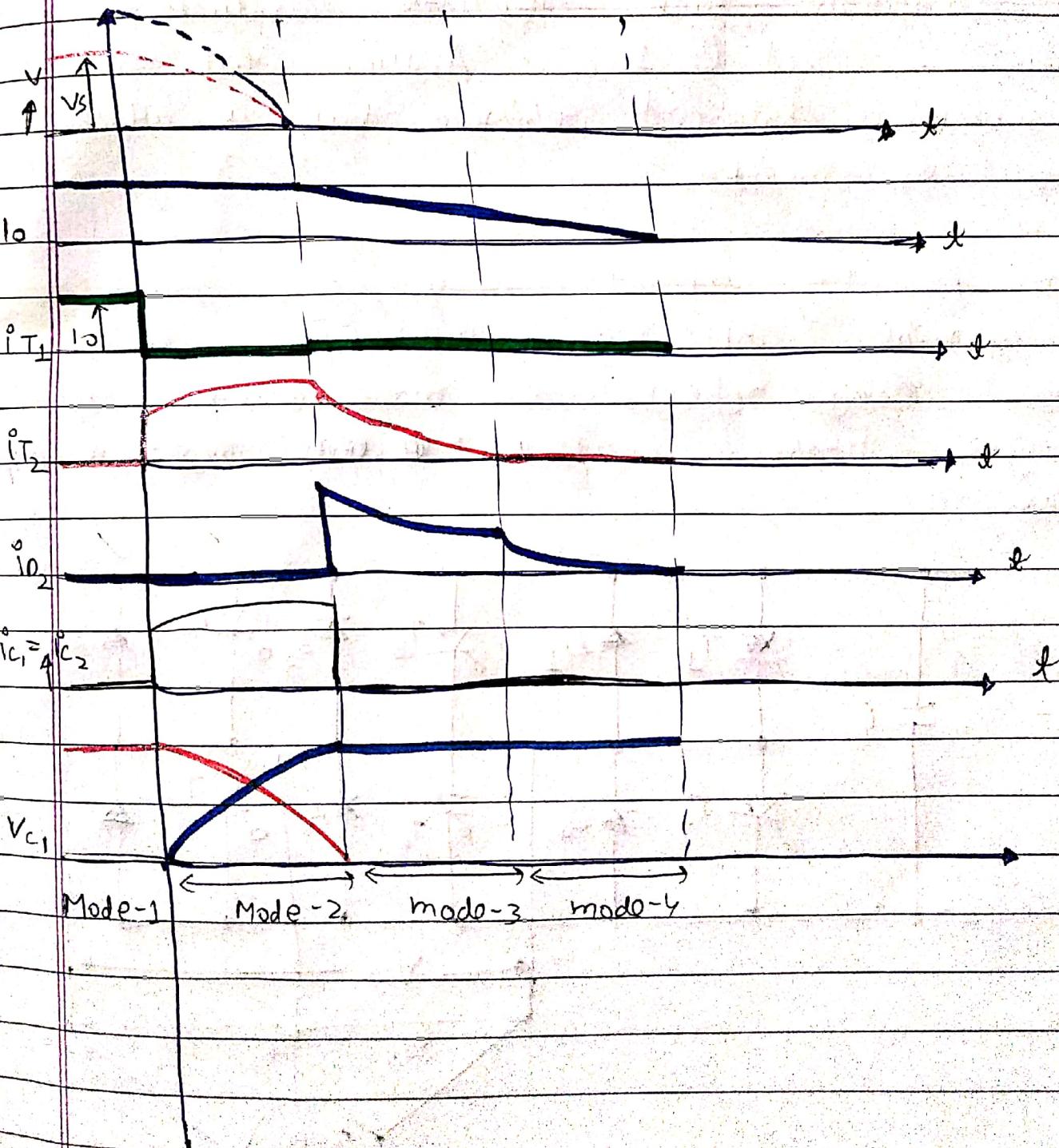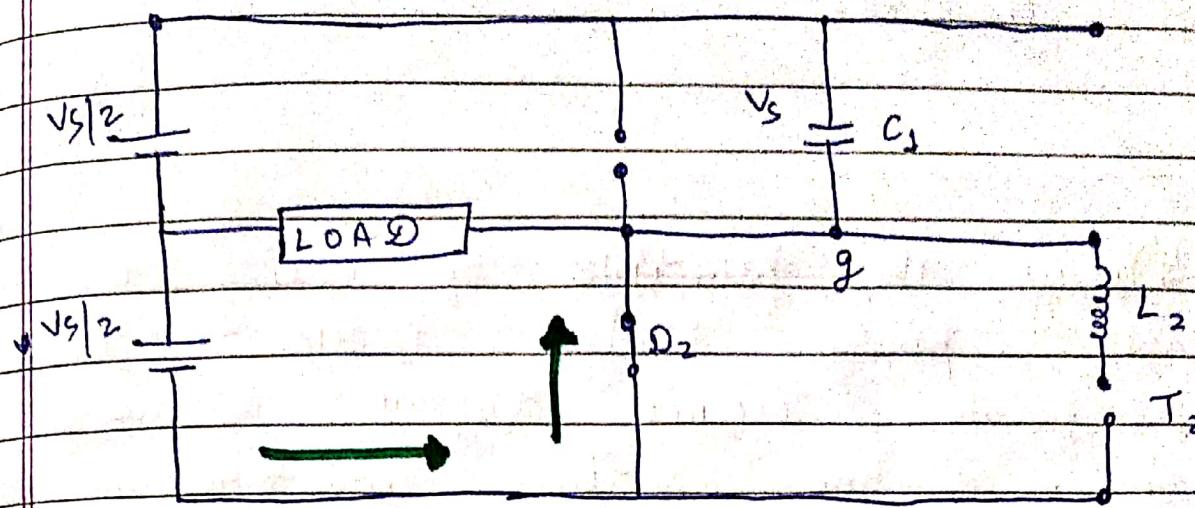

- It uses less number of Thyristors & diodes compared to modified three phase half bridge inverter.



Ques 06 Discuss the principle of working of three phase bridge inverter with appropriate circuit diagram. Draw phase & line voltage waveforms on the assumption each thyristor conducts for (a) 180° and (b) 120° . Assume that star connected balanced resistive load is attached to the inverter.

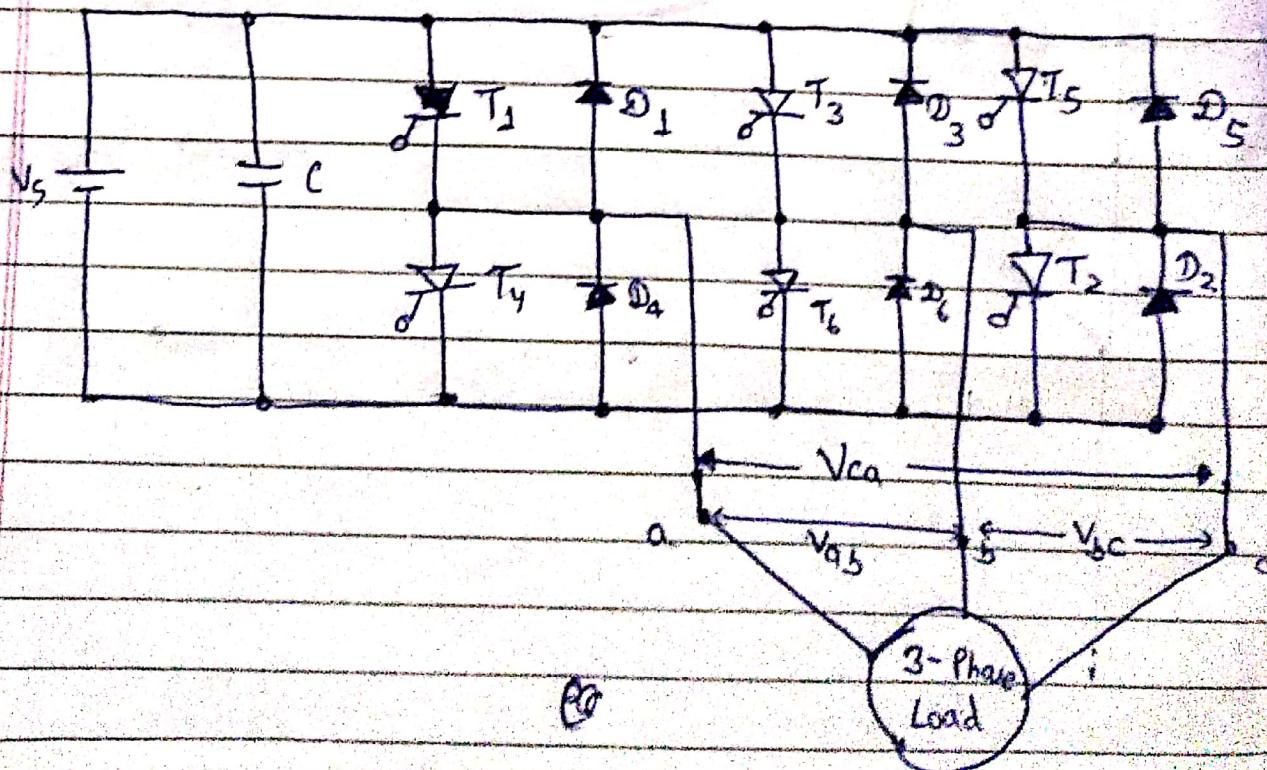This for providing adjustable - frequency power to industrial applications, three phase inverters are more common than single phase inverters.



180° degree

0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°
5,6,1	16,1,2	1,2,3	12,3,4	3,4,5	4,5,6	15,6,1	6,1,2	1,2,3	12,3,4	3,4,5	4,5,6	

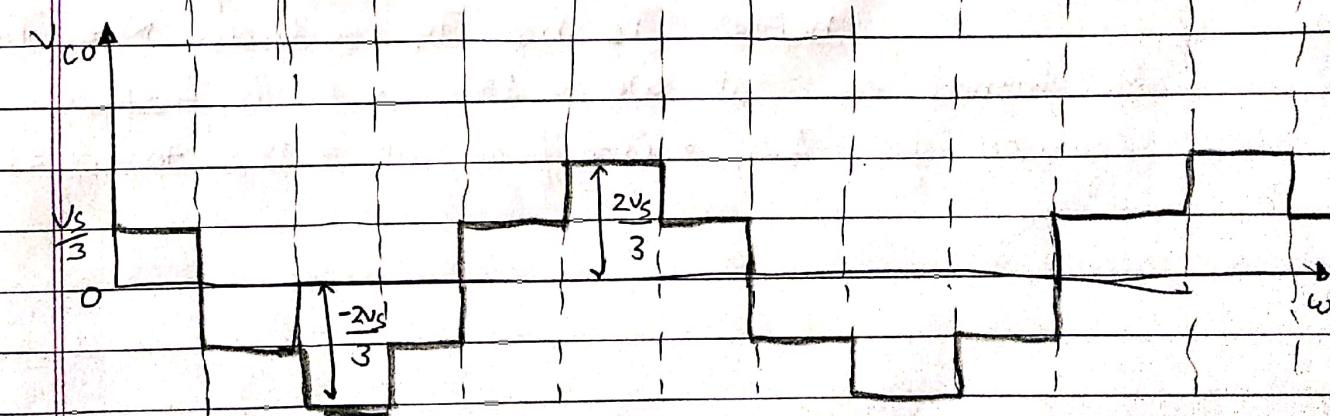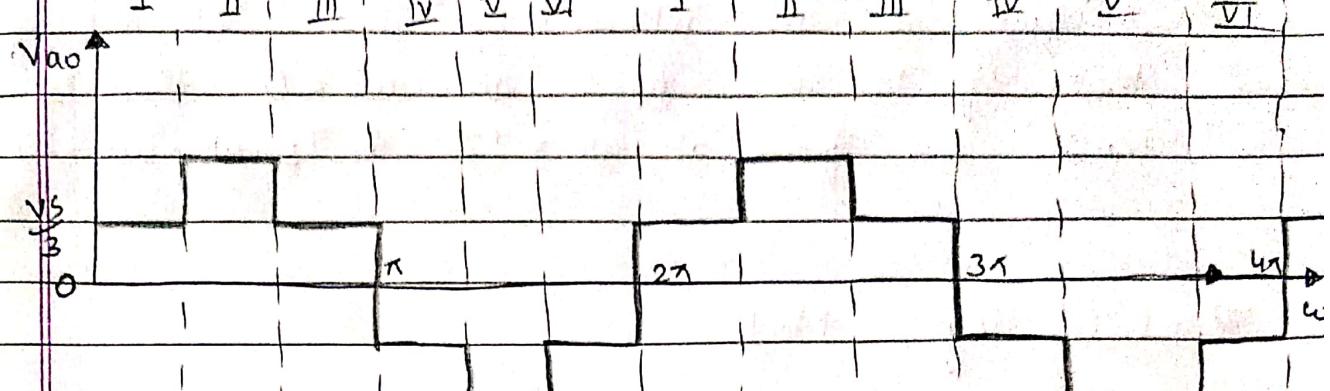


In three phase inverters, each SCR conducts for 180° of a cycle. Thyristor pairs in each arm i.e., T_1, T_4 ; T_3, T_6 & T_5, T_2 are turned on with a time interval of 180° .

from waveform: T_1 conducts for 180° of ωt , for next 120° of a cycle,
thyristor in the upper group i.e. T_2, T_3, T_4 conducts at an interval of 120° . It implies
that if T_1 is fired at $\omega t = 0^\circ$ then T_2
must be fired at $\omega t = 120^\circ$ & T_3 at $\omega t = 240^\circ$

$\Rightarrow 120^\circ$ degree Mode

For 120° degree mode VSI, each thyristor
conducts for 120° of a cycle. Like 180° mode,
 120° mode inverter also requires six steps,
each of 60° duration for completing one cycle of
the o/p ac voltage.

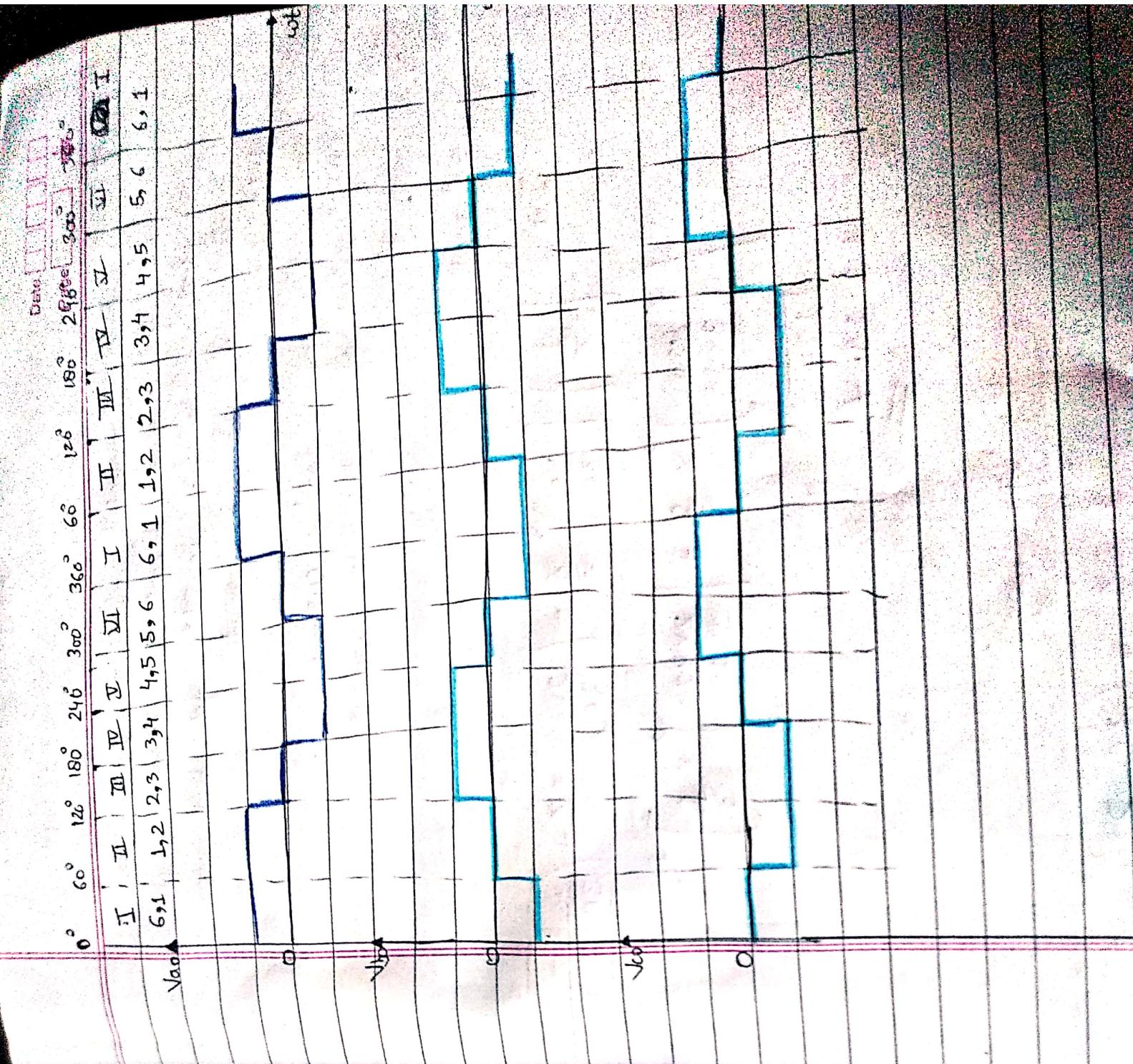from waveform: first row shows that T_1 conducts
for 120° & ~~conducts for next 60°~~
neither T_2 nor T_4 conducts. Now T_4
is turned on at $\omega t = 180^\circ$ and it further
conducts for 120° , i.e. from $\omega t = 180^\circ$ to $\omega t = 300^\circ$



$$87.12 \times \frac{2}{3} + 340.4 \times \frac{1}{3}$$

Date / /
Page

Ques 07 A star connected load of 15Ω per phase is fed from $420V$ DC source through 3-phase bridge inverter for both (a) 180° mode & (b) 120° mode.

determine:

- (i) rms value of load current
- (ii) rms value of thyristor current
- (iii) load power

(a) 180° mode.

$$I_{\text{load}} = \left[\frac{1}{\pi} \left\{ \left(\frac{v_s}{3R} \right)^2 \frac{\pi}{3} + \left(\frac{2v_s}{3R} \right)^2 \times \frac{\pi}{3} + \left(\frac{v_s}{3R} \right)^2 \frac{\pi}{3} \right\} \right]^{1/2}$$

$$= \left[\left(\frac{420}{3 \times 15} \right)^2 \times \frac{2}{3} + \left(\frac{2 \times 420}{3 \times 15} \right)^2 \times \frac{1}{3} \right]^{1/2}$$

$$= \sqrt{174}$$

$$= 13.190 A$$

=

Rms value of thyristor current

$$I_{T1} = \left[\frac{1}{2\pi} \left\{ \left(\frac{420}{3 \times 15} \right)^2 \times \frac{2\pi}{3} + \left(\frac{2 \times 420}{3 \times 15} \right)^2 \times \frac{\pi}{3} \right\} \right]^{1/2}$$

$$= \left[\frac{1}{2\pi} \cdot \frac{\pi}{3} \left\{ \left(\frac{420}{3 \times 15} \right)^2 \times 2 + \left(\frac{2 \times 420}{3 \times 15} \right)^2 \right\} \right]^{1/2}$$

$$= \left[\frac{1}{6} \left\{ \left(\frac{420}{45} \right)^2 \times 2 + \left(\frac{840}{45} \right)^2 \right\} \right]^{1/2}$$

$$= \left[\frac{1}{6} \left\{ 87.12 \times 2 + 340.4 \right\} \right]^{1/2}$$

$$= \sqrt{87}$$

$$= 9.324 \text{ A}$$

Power delivered to Load

$$= 3 I_{\text{av}}^2 R$$

$$= 3 (\sqrt{174})^2 \times 15$$

$$= 7.83 \text{ kW}$$

(b) 120° mode:

$$I_{\text{av}} = \left[\frac{1}{\pi} \left(\frac{210}{420} \right)^2 \times \frac{2\pi}{3} \right]^{1/2}$$

$$= \sqrt{\frac{(14)^2}{3}} \times \frac{1}{2}$$

$$= \sqrt{130.66}$$

~~$$= \sqrt{9.333}$$~~

~~$$= 11.430 \text{ A}$$~~

Rms value of thyristor current

$$I_{T_1} = \left[\frac{1}{2\pi} \left(\frac{210}{420} \right)^2 \times \frac{2\pi}{3} \right]^{1/2}$$

$$= \sqrt{65.33}$$

$$= 0.002 \text{ A}$$

(B) Load power


$$= 3 I^2 R$$

$$= 3 (\sqrt{3} \cdot 6)^2 \cdot 15$$

$$= 5.877 \text{ kW}$$

Ques 08 Discuss Sinusoidal pulse modulation as used in PWM Inverters?

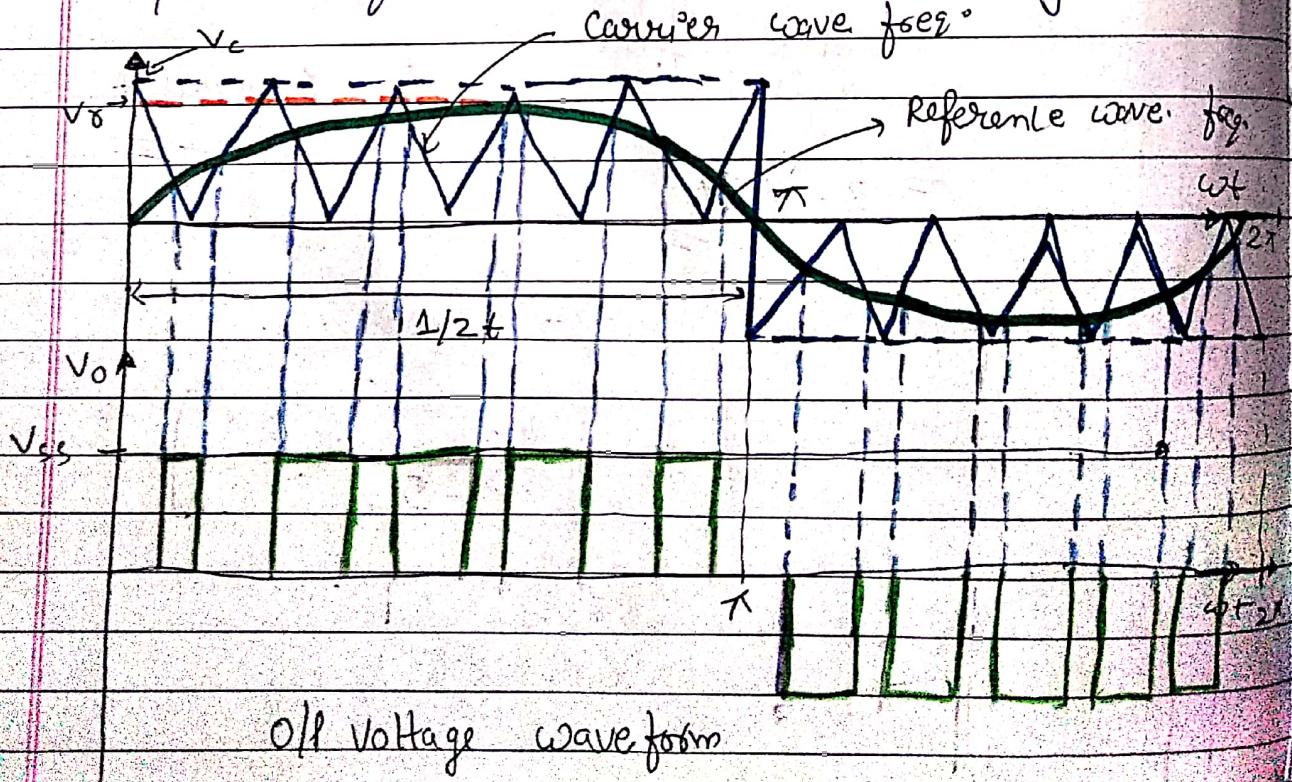In this method of modulation, several pulses per half cycle are used as in the case of multiple-pulse modulation (MPM). In MPM, the pulse width is equal for all the pulses. But in SPM, the pulse width is a sinusoidal funcⁿ of the angular position of the pulse in a cycle.



for realizing Sime's a high-freq. triangular carrier wave V_c is compared with a sinusoidal reference wave V_r of desired freq.

The intersection of V_c & V_r waves determines the switching instants and commutation of the modulated pulse. V_c is the peak value of triangular carrier wave and V_r that of the reference, or modulating signal.

The carrier & reference waves are mixed in a comparators. When sinusoidal wave has magnitude higher than the triangular wave, the comparator o/p is high, otherwise it is low.