
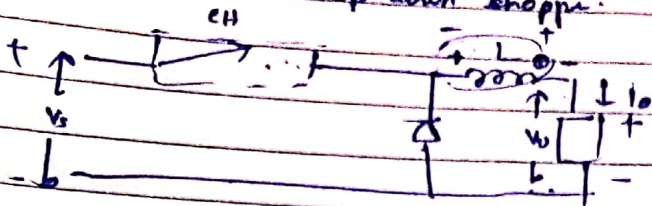


Step down chopper.

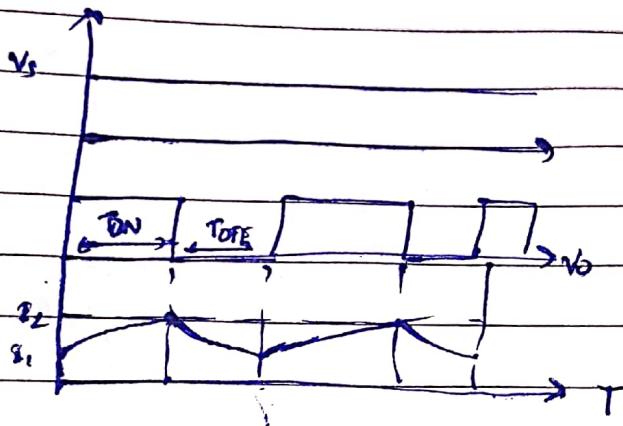

CH OFF $V_o = 0$ - cor 0

CH ON $V_o = V_s$



energy concept

$$V_s + L = V_o \quad V_s + L = V_o$$

$$L = V_o - V_s \quad V_s - L = V_o$$

$$L = V_o - V_s \quad V_s - L = V_o$$

$$(V_o - V_s) \times \frac{L + L_2}{2} \times T_{ON} = \frac{(L + L_2)}{2} \times V_o \times T_{OFF}$$

$$L - V_o = 0 \quad V_o \times T_{OFF}$$

$$V_o \times T_{ON} = V_o \times T$$

$$V_o = V_s \times \frac{T}{T}$$

$$(V_s - V_o) \times \frac{L + L_2}{2} \times T_{ON} = \frac{(L + L_2)}{2} \times V_o \times T_{OFF}$$

$$= (V_o) \times \frac{L + L_2}{2} \times T_{OFF}$$

$$V_s \times T_{ON} = V_o \times T$$

$$V_o = V_s \times \frac{T_{ON}}{T}$$

Conserving energy in the inductor at both time during T_{ON} and T_{OFF}

$$(V_s - V_o) \times \left(\frac{L + L_2}{2} \right) \times T_{ON} = V_o \times \left(\frac{L + L_2}{2} \right) \times T_{OFF}$$


$$T_{ON} \times V_s = V_o \times T$$

$$V_o = V_s \times \frac{T_{ON}}{T}$$

$V_o = V_s \times D$ duty cycle can be varied to get the necessary voltage


Step up chopper:

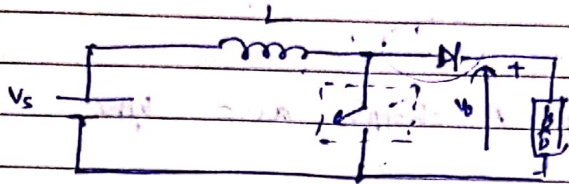The avg. V_o is a step up chopper $> (V_s)$. The figure below shows a configuration of a step up chopper.



current and voltage waveforms.

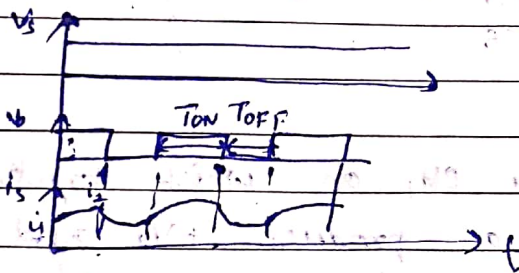V_o is +ve when chopper is switched on and -ve when chopper is off



where T_{ON} - time interval when chopper is on

T_{OFF} - time interval when chopper is off.

V_L - Load Voltage.

Assuming that the energy in the conductor will not change during on and off state so:

$$E_{ON} = V_L I_L t$$

$$= V_L (i_1 + i_2) \times t$$

$$E_{ON} = V_s \times T_{ON} (i_1 + i_2)$$

$$E_{OFF} = (V_o - V_s) \times T_{OFF} \times \frac{(i_1 + i_2)}{2}$$

$I_L = \frac{i_1 + i_2}{2} \Rightarrow$ average current across L

$V_L = V_s$ during on state

$$\alpha = \frac{T_{ON}}{T_{OFF}}$$

$\alpha = \text{duty}$

$$V_s \times T_{ON} = (V_o - V_s) \times T_{OFF}$$

Good Write $V_s (T_{ON} + T_{OFF}) = V_o \times T_{OFF}$
 $V_o = V_s \frac{T_{ON} + T_{OFF}}{T_{OFF}}$

$$V_o = V_s (1 + \alpha)$$

$$V_o \geq V_s$$

$$\alpha = 0$$


$$\alpha = 1$$

Two quadrant chopper:

In a 2 quadrant chopper, 2 different types of chopper are connected in parallel.

For eg. Type - C chopper:

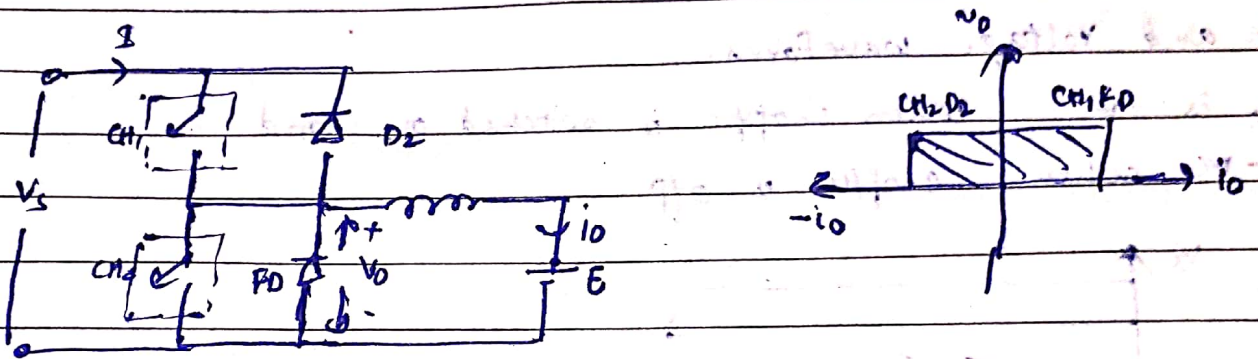
It is made by connecting type A chopper and type B chopper in parallel.



First when we make the CH_1 on which together with FD produce a produce $+V_o$ and $+i_o$

Next when we make the CH_1 off and CH_2 on it acts like a type - B chopper and produce a $+V_o$ and $-i_o$, which gives us the 2 quadrant chopper.


Four Quadrant chopper

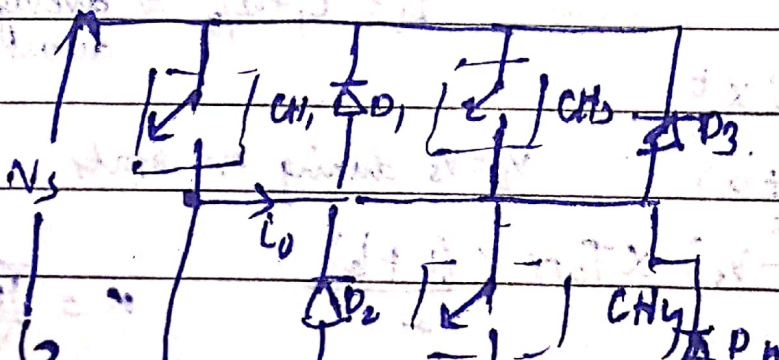


• **First Quadrant:** During the first quadrant operation the chopper CH_1 will be on. Chopper CH_2 will be off and CH_1 will be operated. As the CH_1 and CH_2 is on the load voltage V_o will be equal to source voltage V_s and $I_L = I_o$ will begin to flow. V_o is the and I_o is the.

• **Second Quadrant:** In this case CH_2 will be operation and other 3 are kept off. As CH_2 is on negative current will start flowing through the inductor L . When CH_2 is off the current will be fed back to source through the diodes D_1 and D_2 . The $E + L \frac{di}{dt}$ will be more than source voltage V_s .

Similarly: 3rd and 4th quadrant will function as to give the following graph

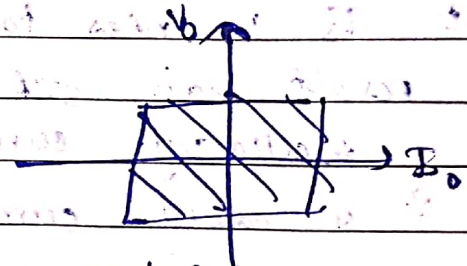

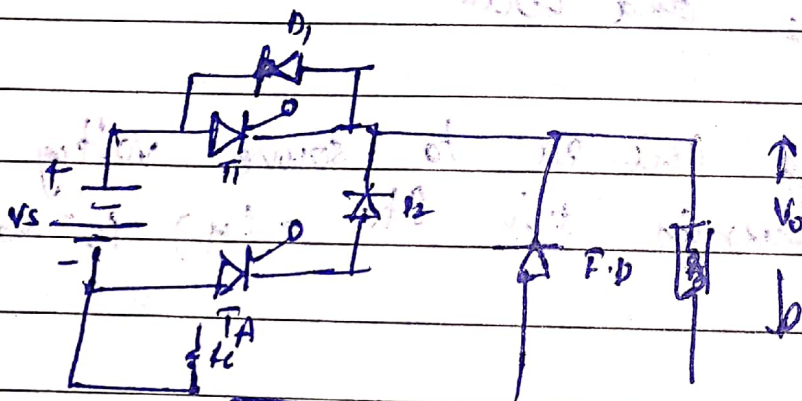Ques 6) Explain the working of current commutated chopper. Also draw its associated waveform.



Capacitor is charged to V_s , min thyristor T_1 is fired at $t = 0$, so the load voltage $V_o = V_s$

At $t = t_1$, auxiliary thyristor is turned on commutating main thyristor.

Within turning on of a TA, an oscillation current i_c is set up in the ext.

$$i_c = \frac{V_s}{\omega L} \sin \omega t = V_s \sqrt{\frac{C}{L}} \sin \omega t$$

At t_2 , $V_c = -V_s$ & i_c tends to reverse in the auxiliary thyristor (TA), it gets naturally commutated.

As TA is reverse biased & turns off at t_2 oscillatory current i_c begins to flow through C, L, D_2 & T_1 .

At T_3 i_c rises to I_0 so that $i_{T_1} = 0$. As a result main SCR T_1 is turned off at T_3 . Since oscillatory current through T_1 turns it off, it is called current commutation app.

After t_4 , a constant current equal to I_0 flows through V_s, C, L, D_2 and Load.

Capacitor C is charged due to source voltage V_s at t_3 , so during t_{in} ($t_3 - t_4$) $i_c = I_0$.

Numerical Ques: 09

Q9)

Solⁿ : $E_0 = 5V$

a) $E_{A \text{ max}} = 13.5$, $E_{d1 \text{ min}} = 10V$

$$M = \frac{E_0}{E_{dc}} = \frac{T_{on}}{T}$$

$$T_{on} = \frac{E_0}{E_{dc} \times 1F} = \frac{5}{10 + 50 \times 10^3}$$

max period = $10 \mu \text{ sec}$

b) $E_0 = 10A$

the d/p pow II I_c

$$E_{dc} \cdot I_c = E_0 \cdot I_0$$

$$12 \times I_c = 5 \times 10$$

$$I_c = 4.16$$

c) $I_L = 500mA$

$$A = \frac{5(10-5)}{1 \times 10^3 \times 10 \times 500 \times 10^{-3}} = 100 \mu m$$

Q10) $E_{dc} = 200V$, load am = $I_0 = 50A$ & $t_q = 20 \mu s$

① $C \geq \frac{\pi}{2} \frac{t_q}{E_{dc}} I_0 \geq \frac{\pi}{2} \frac{200 \times 10^{-6} \times 50}{200} \geq 78.5 \mu F$

capacitor voltage rating = safety factor $\times E_{ac}$
 $= 1.5 \times 200 = 300V$

(i) selection of inductor L_1

$$t_{on} = \sqrt{L_1 C}$$

$$L_1 = \frac{(t_{on})^2}{C} = \frac{200 \times 200 \times 10^{-12}}{2.8 \times 10^{-6}} = 0.51$$

$$L_1 = L_2 = 0.51 \text{ mH}$$

(ii) selection of scf T_1

$$V_{BO} = \text{safety factor} \times E_{de} = 1.5 \times 200 = 300 \text{ V}$$

$$I_T = I \quad I \times r_o = 1.5 \times 50 = 750$$

(iv) selection of auxiliary scf T_2

$$t_{on} \text{ off } t_{in} = t_{on} \leq \frac{\pi}{2} \sqrt{L_1 C} \leq \frac{\pi}{2} \sqrt{0.51 \times 10^{-3} \times 2.8 \times 10^{-6}}$$

$$t_{on} \approx 250 \text{ us}$$

(v) selection of Diode D_1

$$\text{PIV rating of diode} = V_{BO} \text{ of scf} = 300 \text{ V}$$

$$I_D = I_T = 75 \text{ A}$$

(vi) scf dynamic character

$$\text{Main scf } T_1 \quad \frac{dV}{dt} = \frac{V_{omax}}{C}$$

$$= \frac{50}{2.8 \times 10^{-6}}$$

$$= 0.64 \text{ V/us}$$

$$\frac{dI}{dt} = \frac{E_{Rpn}}{L_1}$$

$$\leq \text{safety factor} \times \frac{I_{Rpn} \times E_{ac}}{L} = 0.59 \text{ A/us}$$

Good Write

$$T_2 = \frac{dv}{dt} = \frac{E_{peak}}{\sqrt{L_1 C}} \quad \text{--- B.O}$$

$$= 1.49 \mu s$$

$$\frac{di}{dt} = \frac{E_{peak}}{L} = \frac{1.5 \times 100}{2 \mu H} = 150 A/\mu s$$