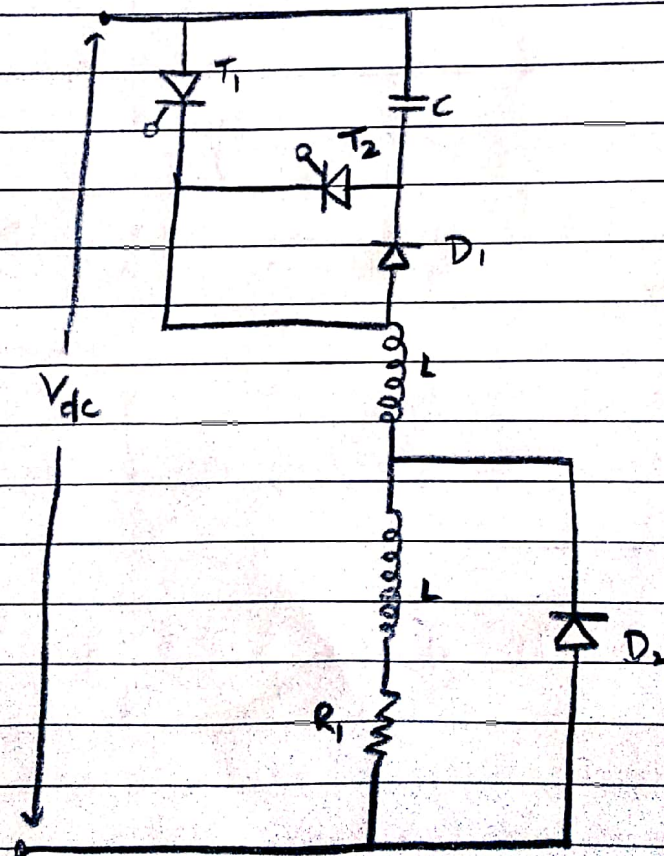


Ques:07 Mention the advantages of Jones Chopper over other chopper circuits.

Ans: Jones Chopper is an example of class D commutator in which charged capacitor is switched by an auxiliary SCR to commutate the main SCR. In this circuit SCR1 is the main switch & SCR2 is the auxiliary switch which is lower capacity than SCR1 & is used to commutate SCR1 by a reverse voltage developed across the capacitor C.






## Advantages :

- \* It allows the use of higher voltage and lower microfarad commutating capacitors. This is because the trapped energy of inductor  $L_2$  can be forced in to the commutating capacitor rather than simply charging the capacitor by supply voltage.
- In this circuit there is no starting problem & anyone of the SCR can be turned on initially there is great flexibility in control also.



Ques:08 Describe Morgan chopper with associated voltage & current waveforms.

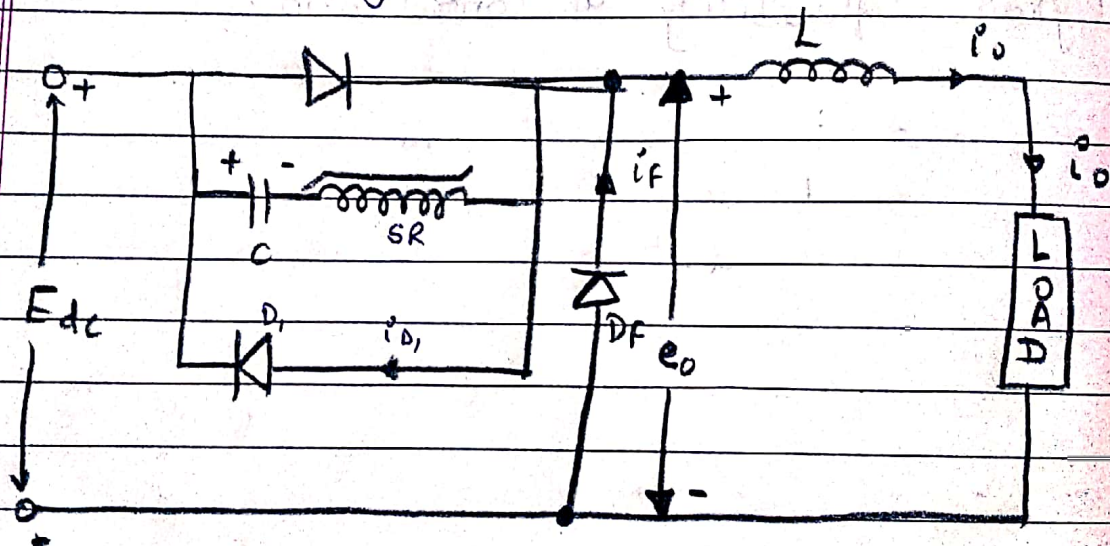Ans: Figure shows the power-circuit of Morgan chopper. In this circuit,  $T_1$  is the main thyristor, whereas capacitor  $C$ , saturable reactor  $SR$  and diode  $D_1$  forms the commutating circuit. The exciting current of the saturable reactor is assumed to be negligible small. When the saturable reactor is saturated it has very low inductance.



when the SCR  $T_1$  is OFF, capacitor  $C$  will charge to the supply voltage  $E_{dc}$  with the polarity as shown in figure. And the saturable reactor is placed in the positive saturation condition. The capacitor charging path is

$$E_{dc} \rightarrow C \rightarrow SR \rightarrow \text{Load} \rightarrow E_{dc}$$



Thyristor  $T_1$  is triggered at time  $t = t_1$ .  
 When thyristor  $T_1$  is turned on, the  
 Capacitor Voltage appears across the  
 saturable reactor & the core flux is  
 driven from the positive saturation towards  
 negative saturation.

