

DC/AC Converter

Part-1

By: Dr. Bhavnes Kumar
Assistant Professor

DC/AC Converter: Inverter

- ▶ A device that converts dc power into ac power at a desired output voltage and frequency
- ▶ The DC source may be in the form of batteries, generators, solar cells or for large power applications, controlled or uncontrolled ac-dc rectifier circuits.
- ▶ The configuration of AC/DC converter and DC/AC converter is called a dc-link converter.
- ▶ Applications:
 - ▶ Emergency lighting systems
 - ▶ Uninterrupted power supplies
 - ▶ AC motor drives

Classifications

▶ On the basis of input source

- ▶ **Voltage Source Inverter (VSI)** : Have stiff dc voltage source at the input, in other words it have dc voltage source with negligible impedance.
- ▶ **Current Source Inverter (CSI)**: Have stiff current source at the input in other words dc source have high impedance.

▶ On the basis of Commutation

- ▶ **Line commutated Inverters**: Can't function as isolated ac voltage source or as a variable frequency generator with dc power at the input.
- ▶ **Forced commutated Inverters**: Can provide an independent ac output voltage of adjustable voltage and adjustable frequency.


▶ On the basis of output

- ▶ Single phase Inverters
- ▶ Three phase Inverters

Single phase VSIs


► Single phase half bridge

Single Leg

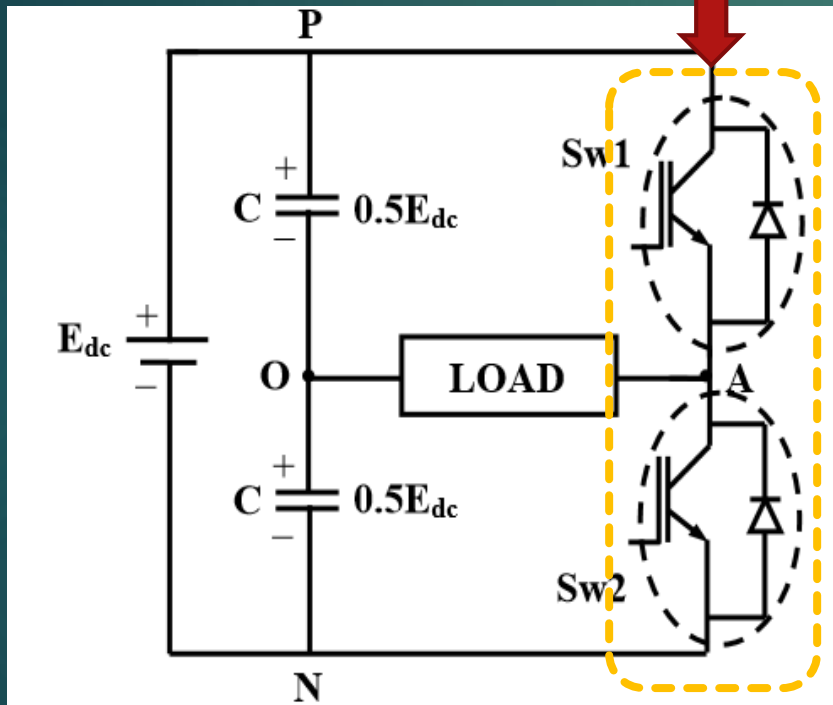

► Single phase full bridge


Two Legs

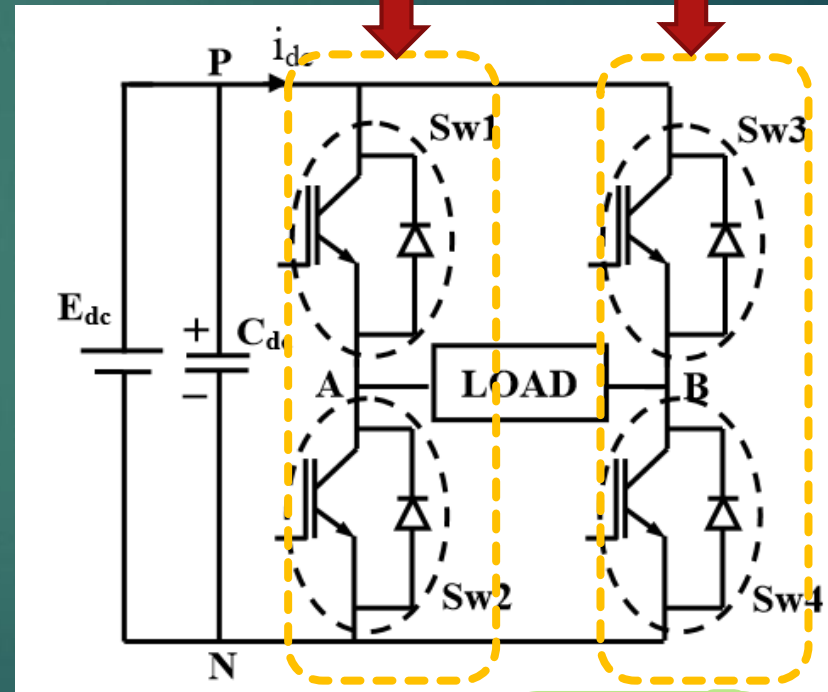

First generation inverters, using thyristor switches, were almost invariably square wave inverters because thyristor switches could be switched on and off only a few hundred times in a second


Single phase half bridge VSI

- ▶ In half bridge topology the input dc voltage is split in two equal parts through an ideal and loss-less capacitive potential divider.
- ▶ Each leg of the inverter consists of two series connected electronic switches
- ▶ Each of these switches consists of an IGBT type controlled switch across which an uncontrolled diode is put in anti-parallel manner
- ▶ These switches are capable of conducting bi-directional current but they need to block only one polarity of voltage
- ▶ In half bridge topology the single-phase load is connected between the mid-point of the input dc supply and the junction point of the two switches
- ▶ the switches should neither be simultaneously on nor be simultaneously off. Simultaneous turn-on of both the switches will amount to short circuit across the dc bus and will cause the switch currents to rise rapidly.

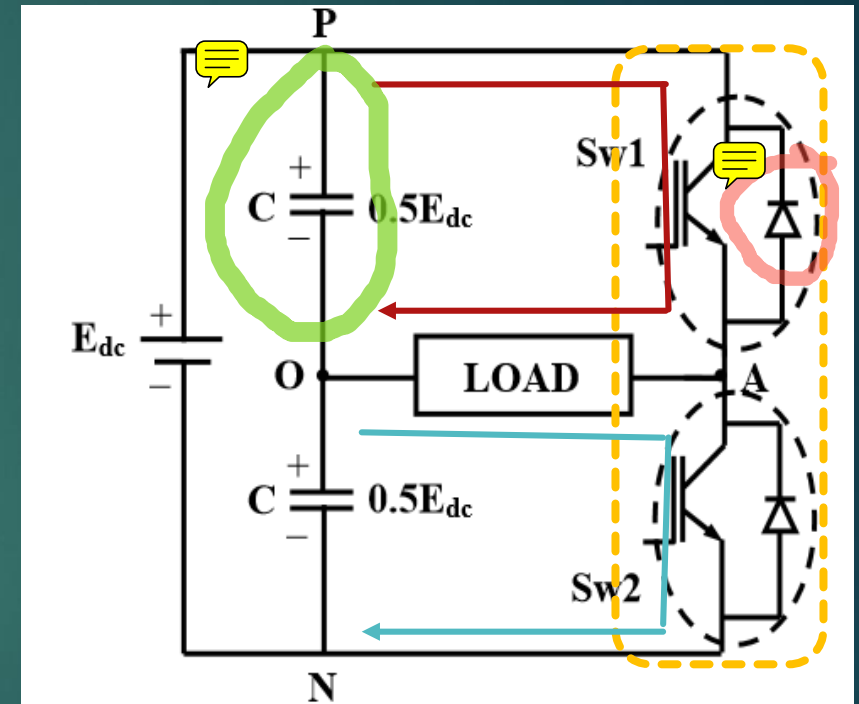

For Resistive load

- ▶ The switching sequence is to design that switch SW_1 is on for the time duration $0 \leq t \leq T_1$ and the switch SW_2 is on for the time duration $T_1 \leq t \leq T_2$.
- ▶ When switch SW_1 is turned **ON**, the instantaneous voltage across the load is
$$V_o = +E_{dc}/2$$
- ▶ When the switch SW_2 is only turned **ON**, the voltage across the load is
$$V_o = -E_{dc}/2$$
- ▶ The waveform of the output voltage and the switch currents for a resistive load is shown in Fig.

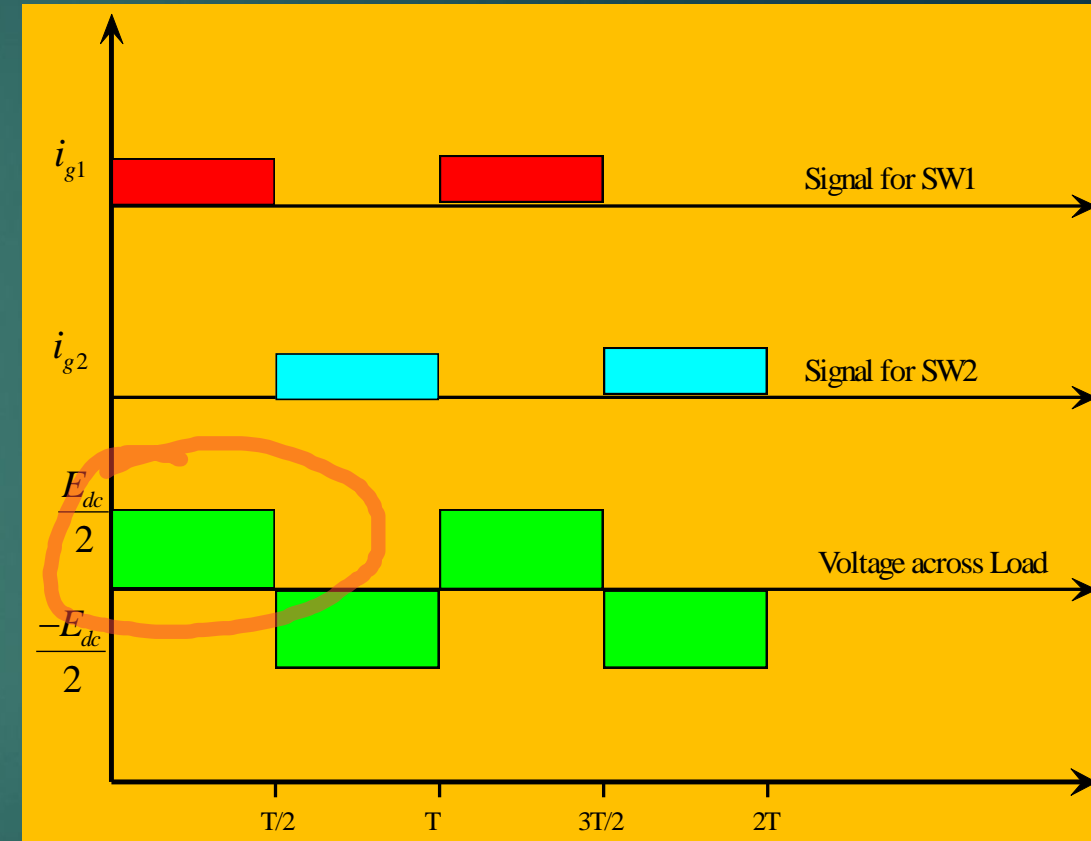

The r.m.s. value of output voltage v_o is given by : $V_o, rms = \frac{1}{T_1} \int_0^{T_1} \frac{E_{dc}^2}{4} dt = \frac{E_{dc}}{2}$

The instantaneous output voltage (v_o) is rectangular in shape. The instantaneous output can be expressed in Fourier series as:

$$v_o = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b_n \sin(n\omega t)$$

Due to the quarter wave symmetry along the time axis (Figure 3), the values of a_0 and a_n are zero. The value of b_n is given by:

$$b_n = \frac{1}{\pi} \left[\int_{-\frac{\pi}{2}}^0 \frac{-E_{dc}}{2} d(\omega t) + \int_0^{\frac{\pi}{2}} \frac{E_{dc}}{2} d(\omega t) \right] = \frac{2E_{dc}}{n\pi}$$

Substituting the value of b_n :

Output voltage
$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{2E_{dc}}{n\pi} \sin(n\omega t)$$

Output current
$$i_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{R} \frac{2E_{dc}}{n\pi} \sin(n\omega t)$$


For $n=1$

$$v_{o1} = \sum \frac{2E_{dc}}{\sqrt{2}\pi} \approx 0.45E_{dc}$$



Single phase full bridge VSI with R Load

► Operation

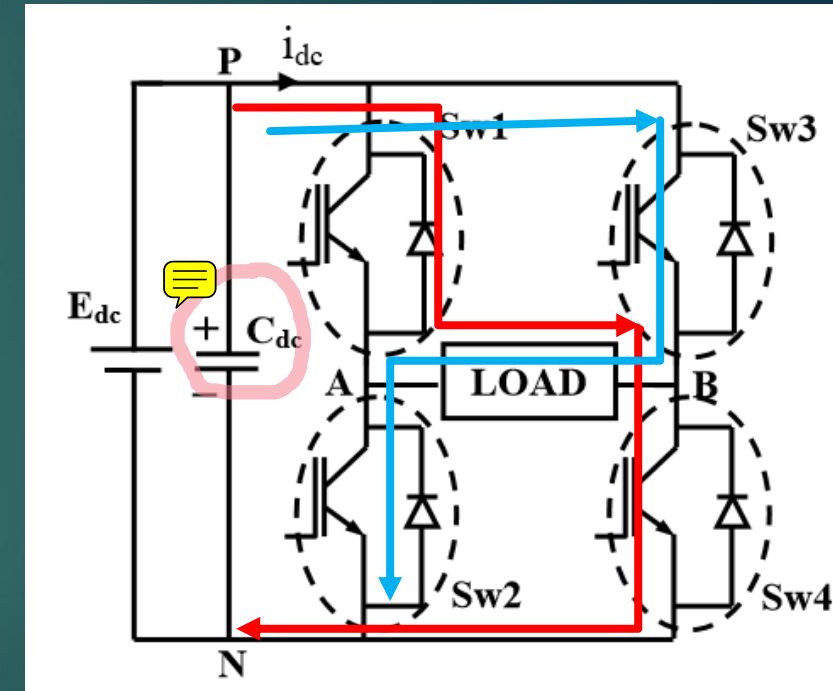- Switch SW1 and SW4 are turned ON simultaneously for half of the time period
 - Path of current flow is marked with red color line arrow
- Switch SW2 and SW3 are turned ON simultaneously for the remaining half cycle.
 - Path of the current flow is marked with blue color line arrow.



Firing Scheme

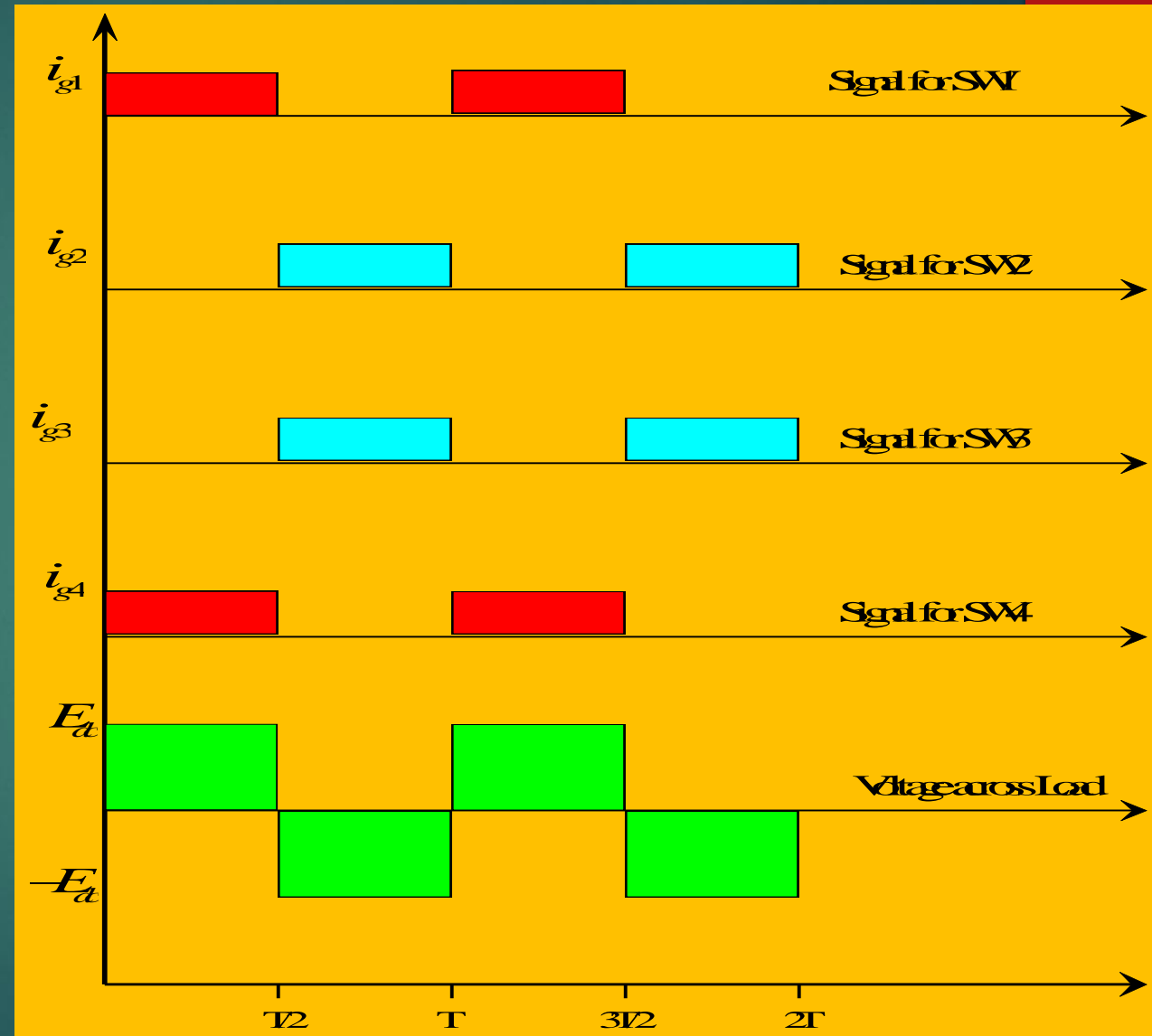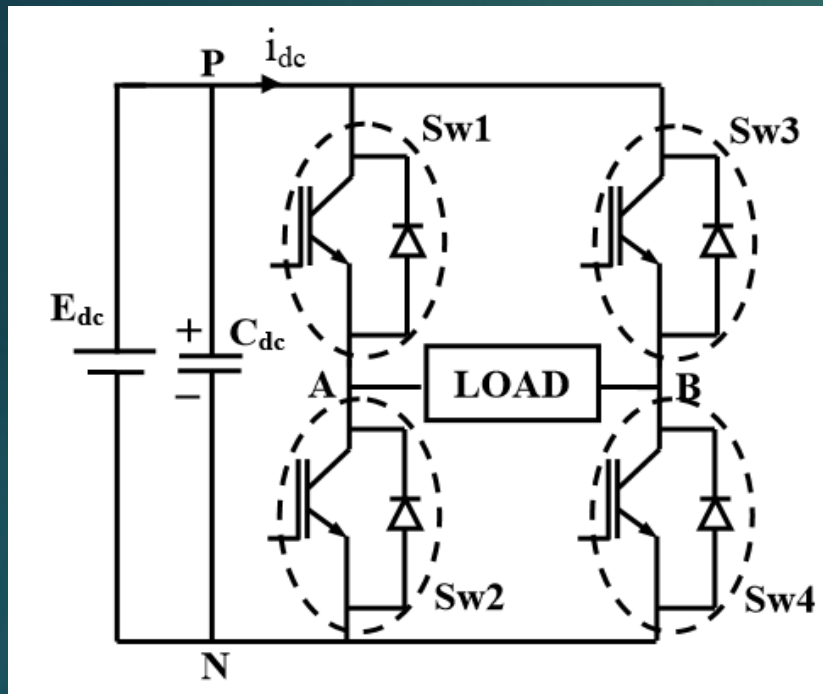



Thank You